

EXPERIMENT No-5

Aim: To Design a Half Adder and Full Adder using VHDL

Description:

Half adder


Half adder is a combinational arithmetic circuit that adds two numbers and produces a sum bit (S) and carry bit (C) as the output. If A and B are the input bits, then sum bit (S) is the X-OR of A and B and the carry bit (C) will be the AND of A and B.

The sum and carry are as follows:

$$\text{Sum} = A'B + AB' = A \oplus B$$

$$\text{Carry} = AB$$

 The truth table, schematic representation and XOR//AND realization of a half adder are shown in the figure below.



Full adder


The full adder is used to add three 1-bit binary numbers A, B, and carry C. The full adder has three input states and two output states i.e., sum and carry.

Sum:

- Perform the XOR operation of input A and B.
- Perform the XOR operation of the outcome with carry. So, the sum is $(A \text{ XOR } B) \text{ XOR } C_{in}$ which is also represented as: $(A \oplus B) \oplus C_{in}$.

Carry:

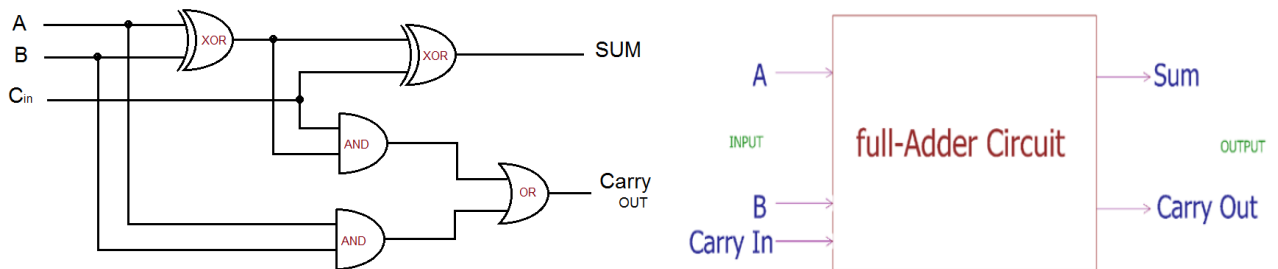- Perform the 'AND' operation of input A and B.
- Perform the 'XOR' operation of input A and B.
- Perform the 'OR' operations of both the outputs that come from the previous two steps. So the 'Carry' can be represented as: $A.B + (A \oplus B)$



Inputs			Outputs	
A	B	C_{in}	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Program:

--Half adder

```

library ieee ;

use ieee.std_logic_1164.all ;

entity half_adder is

port ( a, b : in std_logic ;

s, c : out std_logic ) ;

end half_adder ;

architecture dataflow_half of half_adder is

begin

s <= a xor b;

c <= a and b;

end dataflow_half;

```

Program:

--Full Adder

1. VHDL code for full adder data flow:

```

library ieee ;

use ieee.std_logic_1164.all ;


entity fa is

Port ( a : in std_logic;

b : in std_logic;

cin : in std_logic;

s : out std_logic;

```

```

cout : out std_logic);

end fa;

architecture Behavioral of fa is

begin

s <= (a xor b) xor cin;

cout <= (a and b) or (b and cin) or (a and cin);

end Behavioral;

```

2. VHDL code for full adder behavioral:

```

library ieee;

use ieee.std_logic_1164.all;

use ieee.std_logic_arith.all;

use ieee.std_logic_unsigned.all;

entity fa1 is

Port ( a,b,ci : in std_logic;

s,co : out std_logic

);

end fa1;

```

```

architecture Behavioral of fa1 is

begin

process (a,b,ci)

begin

s<=a xor b xor ci;

```

```
co<=(a and b)or (b and ci)or (ci and a);
```

```
end process;
```

```
end Behavioral;
```

Output:

Half Adder:

Full Adder: