

EXPERIMENT No-9

Aim: To Design an Encoder and Decoder using VHDL


Encoder:

An encoder is a combinational circuit that converts binary information in the form of a 2^N input lines into N output lines, which represent N bit code for the input. For simple encoders, it is assumed that only one input line is active at a time.

4:2 Encoder

Let 4 to 2 Encoder has four inputs Y_3 , Y_2 , Y_1 & Y_0 and two outputs A_1 & A_0 . At any time, only one of these 4 inputs can be '1' in order to get the respective binary code at the output.

Block diagram

 


Truth Table

Inputs				Outputs	
Y_3	Y_2	Y_1	Y_0	A_1	A_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

Boolean functions for each output as: $A_1 = Y_3 + Y_2$, $A_0 = Y_3 + Y_1$

Circuit diagram

 

VHDL program for 4 to 2 encoders:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity encod1 is
Port (a: in STD_LOGIC_VECTOR (3 downto 0);
q:out STD_LOGIC_VECTOR (1 downto 0));
end encod1;
architecture Behavioral of encod1 is
begin
q<="00" when a="0001" else
"01" when a="0010" else
"10" when a="0100" else
"11";
end Behavioral;
```

VHDL program for 8 to 3 encoder:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity encoder is
Port (i: in STD_LOGIC_VECTOR (7 downto 0); y: out
STD_LOGIC_VECTOR (2 downto 0));
end encoder;
```

```
architecture Behavioral of encoder is begin
with i select
y<="000" when "00000001",
"001" when "00000010",
"010" when "00000100",
"011" when "00001000",
"100" when "00010000",
"101" when "00100000",
"110" when "01000000",
"111" when others;
end Behavioral;
```

Output:

Decoder:


A decoder is a device which does the reverse of an encoder, undoing the encoding so that the original information can be retrieved. The same method used to encode is usually just reversed in order to decode.

Decoder is a combinational circuit that has 'n' input lines and maximum of 2^n output lines.

2 to 4 Decoder

Let 2 to 4 Decoder has two inputs A_1 & A_0 and four outputs Y_3 , Y_2 , Y_1 & Y_0 .

Block diagram

 

One of these four outputs will be '1' for each combination of inputs when enable, E is '1'.


Truth table

Enable	Inputs		Outputs			
E	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	x	x	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0

1	1	1	1	0	0	0
---	---	---	---	---	---	---

Boolean functions for each output as $Y_3 = E \cdot A_1 \cdot A_0$, $Y_2 = E \cdot A_1 \cdot A_0'$, $Y_1 = E \cdot A_1' \cdot A_0$, $Y_0 = E \cdot A_1' \cdot A_0'$

Circuit diagram

 

VHDL Program for 2:4 decoder:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity decoder is
Port ( en : in STD_LOGIC;
s : in STD_LOGIC_VECTOR (1 downto 0);
z : out STD_LOGIC_VECTOR (3 downto 0));
end decoder;
architecture arch of decoder is
signal p,q : STD_Logic;
begin
p <= not s(1);
q <= not s(0);
z(0) <= p and q;
z(1) <= p and s(0);
z(2) <= q and s(1);
z(3) <= s(0) and s(1);

```

end arch;

VHDL Program for 3:8 decoder:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity dec1 is
Port (s:in STD_LOGIC_VECTOR (2 downto 0);
y:out STD_LOGIC_VECTOR (7 downto 0));
end dec1;
architecture Behavioral of dec1 is begin
with sel select y<="00000001" when "000",
"00000010" when "001",
"00000100" when "010",
"00001000" when "011",
"00010000" when "100",
"00100000" when "101",
"01000000" when "110",
"10000000" when "111",
"00000000" when others;
end Behavioral;
```

Output: