 


EXPERIMENT No-10

Aim: 2's Complement Adder-Subtractor using VHDL

Description:

- 4-bit Adder-Subtractor:



- For M=1, subtract, the 2's complement of B is formed by using XORs to form the 1's complement and adding the 1 applied to C0
- For M=0, add, B is passed through unchanged

VHDL program:

```
library ieee;
use ieee.std_logic_1164.all;
entity addsub is
    port( M: in std_logic;
          A,B : in std_logic_vector(3 downto 0);
          S : out std_logic_vector(3 downto 0);
          Cout, OVERFLOW : out std_logic);
end addsub;
```

```

architecture struct of addsub is
  component Full_Adder is
    port( X, Y, Cin : in std_logic;
          sum, Cout : out std_logic);
  end component;
  signal C1, C2, C3, C4: std_logic;
  signal TMP: std_logic_vector(3 downto 0);

```

```

begin

```

```

  TMP(0)<= M xor B(0);
  TMP(1)<= M xor B(1);
  TMP(2)<= M xor B(2);
  TMP(3)<= M xor B(3);
  FA0:Full_Adder port map(A(0),TMP(0),M, S(0),C1);
  FA1:Full_Adder port map(A(1),TMP(1),C1, S(1),C2);
  FA2:Full_Adder port map(A(2),TMP(2),C2, S(2),C3);
  FA3:Full_Adder port map(A(3),TMP(3),C3, S(3),C4);
  OVERFLOW <= C3 XOR C4;
  Cout <= C4;
end struct;

```

Waveforms/Outputs: